

Міністерство освіти і науки України
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних
систем» на тему:

«Поведінковий опис цифрового автомата Перевірка роботи
автомата за допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №8

Виконав: ст. гр. КІ-201 Головка І.О.

Прийняв: ст. викладач каф. ЕОМ Козак Н.Б.

Львів - 2024

Мета роботи: на базі стенда реалізувати цифровий автомат для обчислення значення виразів.

Мій варіант - №8

ВАРІАНТ(КІ-201)	ВИРАЗ
1	$((OP1 + OP2 + 10) * OP2) \ll OP1$
2	$((OP1 \text{ or } OP2) + OP2 + 10) - 3$
3	$((OP2 \text{ and } 5) + OP2 + 10) - OP1$
4	$((OP1 + OP2 + 10) \text{ xor } OP2) - OP1$
5	$((1 \ll OP1) + OP2 + 10) - OP1$
6	$((OP1 + OP2 + 10) - 2) \ll OP2$
7	$((OP1 \ll 2) - OP2) + OP2 + 10$
8	$((OP1 * OP2) \gg 1) + OP1 + 10$

Рис. 1 - скріншот заданого варіанту

Виконання роботи

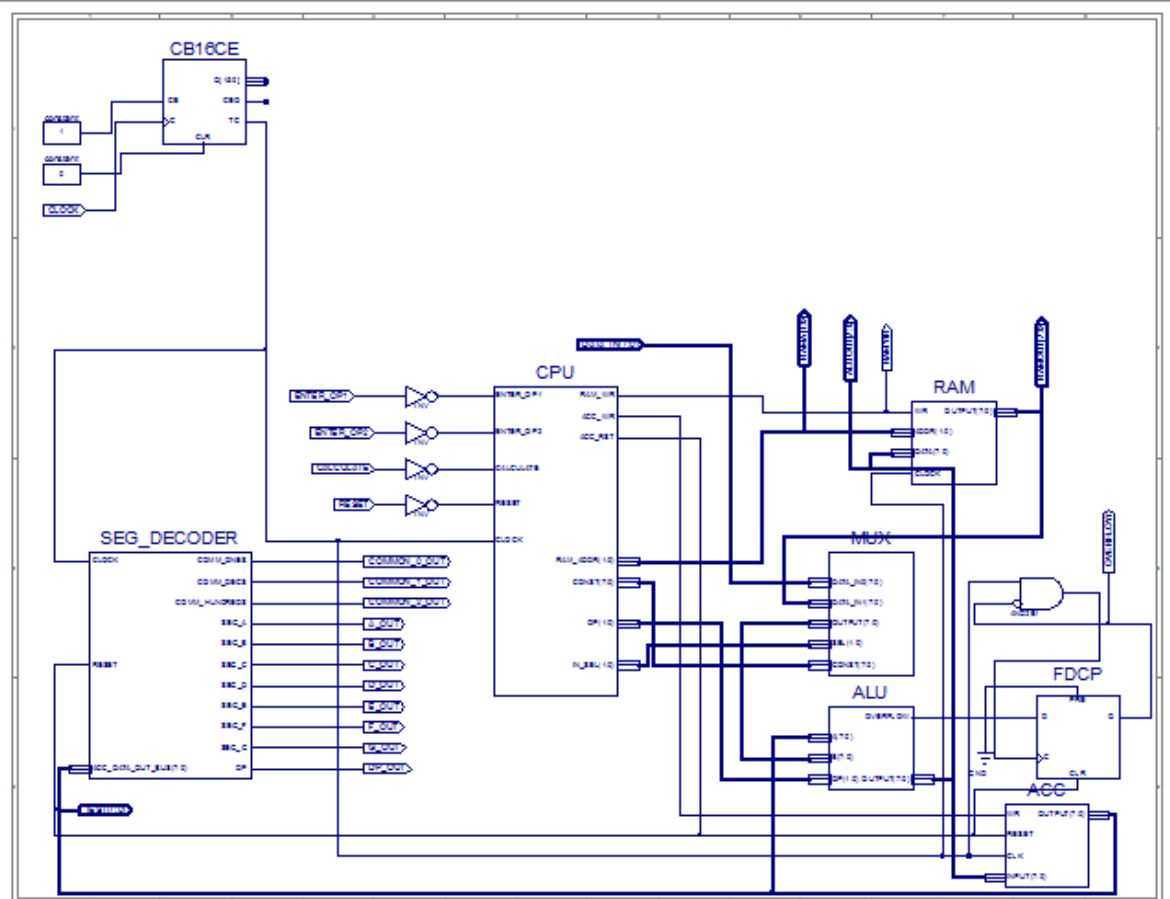


Рис. 2 - Top Level

Файл ACC.vhd:

```
library IEEE;
```

```

use IEEE.STD_LOGIC_1164.ALL;

entity ACC is
    Port ( WR      : in  STD_LOGIC;
          RESET    : in  STD_LOGIC;
          CLK      : in  STD_LOGIC;
          INPUT     : in  STD_LOGIC_VECTOR (7 downto 0);
          OUTPUT    : out STD_LOGIC_VECTOR (7 downto 0));
end ACC;

architecture ACC_arch of ACC is
    signal DATA : STD_LOGIC_VECTOR (7 downto 0);
begin
    process (CLK)
    begin
        if rising_edge(CLK) then
            if RESET = '1' then
                DATA <= (others => '0');
            elsif WR = '1' then
                DATA <= INPUT;
            end if;
        end if;
    end process;

    OUTPUT <= DATA;

end ACC_arch;

```

Файл ALU.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ALU is

```

```

    Port ( A : in  STD_LOGIC_VECTOR(7 downto 0);
          B : in  STD_LOGIC_VECTOR(7 downto 0);
          OP : in  STD_LOGIC_VECTOR(1 downto 0);
          OUTPUT : out STD_LOGIC_VECTOR(7 downto 0);
          OVERFLOW: out STD_LOGIC);
end ALU;

architecture ALU_Behavioral of ALU is
    signal ALUR: STD_LOGIC_VECTOR(15 downto 0) :=
(others => '0');
    signal Carry: STD_LOGIC := '0';
begin
    process(A, B, OP)
    begin
        case (OP) is
            when "01" => ALUR <= ("00000000" & A) +
("00000000" & B);
            when "10" => ALUR <=
std_logic_vector(to_unsigned((to_integer(unsigned(("00000
000" & A))) * to_integer(unsigned(("00000000" &
B))))),16));
            when "11" => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) srl
to_integer(unsigned(B)));
            when others => ALUR <= ("00000000" & B);
        end case;
    end process;
    OUTPUT <= ALUR(7 downto 0);
    OVERFLOW <= ALUR(8) OR ALUR(9) OR ALUR(10) OR
ALUR(11) OR ALUR(12) OR ALUR(13) OR ALUR(14) OR ALUR(15);
end ALU_Behavioral;

```

Файл CPU.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity CPU is
    port( ENTER_OP1 : IN STD_LOGIC;
          ENTER_OP2 : IN STD_LOGIC;
          CALCULATE : IN STD_LOGIC;
          RESET : IN STD_LOGIC;
          CLOCK : IN STD_LOGIC;
          RAM_WR : OUT STD_LOGIC;
          RAM_ADDR : OUT STD_LOGIC_VECTOR(1 DOWNTO
0);

          CONST : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
          ACC_WR : OUT STD_LOGIC;
          ACC_RST : OUT STD_LOGIC;
          IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
          OP : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
end CPU;

architecture CPU_arch of CPU is

    type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2,
RUN_CALC0, RUN_CALC1, RUN_CALC2, RUN_CALC3, RUN_CALC4,
FINISH);
    signal CUR_STATE : STATE_TYPE;
    signal NEXT_STATE : STATE_TYPE;

begin
    SYNC_PROC: process (CLOCK)
    begin
        if (rising_edge(CLOCK)) then
            if (RESET = '1') then
                CUR_STATE <= RST;
            else
                CUR_STATE <= NEXT_STATE;
            end if;
        end if;
    end process;
end CPU_arch;

```

```
        end if;
    end if;
end process;
```

```
    NEXT_STATE_DECODE: process (CLOCK, ENTER_OP1,
ENTER_OP2, CALCULATE)
```

```
    begin
```

```
        NEXT_STATE <= CUR_STATE;
```

```
        case(CUR_STATE) is
```

```
            when RST =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when IDLE =>
```

```
                if (ENTER_OP1 = '1') then
```

```
                    NEXT_STATE <= LOAD_OP1;
```

```
                elsif (ENTER_OP2 = '1') then
```

```
                    NEXT_STATE <= LOAD_OP2;
```

```
                elsif (CALCULATE = '1') then
```

```
                    NEXT_STATE <= RUN_CALC0;
```

```
                else
```

```
                    NEXT_STATE <= IDLE;
```

```
                end if;
```

```
            when LOAD_OP1 =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when LOAD_OP2 =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when RUN_CALC0 =>
```

```
                NEXT_STATE <= RUN_CALC1;
```

```
            when RUN_CALC1 =>
```

```
                NEXT_STATE <= RUN_CALC2;
```

```
            when RUN_CALC2 =>
```

```
                NEXT_STATE <= RUN_CALC3;
```

```
            when RUN_CALC3 =>
```

```
                NEXT_STATE <= RUN_CALC4;
```

```
            when RUN_CALC4 =>
```

```

        NEXT_STATE <= FINISH;
    when FINISH =>
        NEXT_STATE <= FINISH;
    when others =>
        NEXT_STATE <= IDLE;
    end case;
end process;

```

```

OUTPUT_DECODE: process (CUR_STATE)
begin

```

```

    case (CUR_STATE) is
        when RST =>
            RAM_WR <= '0';
            RAM_ADDR <= "00";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when LOAD_OP1 =>
            RAM_WR <= '1';
            RAM_ADDR <= "00";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when LOAD_OP2 =>
            RAM_WR <= '1';
            RAM_ADDR <= "01";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when RUN_CALC0 =>

```

```
RAM_WR <= '0';
RAM_ADDR <= "00";
CONST <= "00000000";
ACC_WR <= '1';
ACC_RST <= '0';
IN_SEL <= "01";
OP <= "00";
when RUN_CALC1 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "10";
when RUN_CALC2 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000001";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "11";
when RUN_CALC3 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "01";
when RUN_CALC4 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00001010";
    ACC_WR <= '1';
```



```

        ACC_RST <= '0';
        IN_SEL <= "10";
        OP <= "01";
    when IDLE =>
        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";
    when others =>
        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";
    end case;
end process;
end CPU_arch;

```

Файл MUX.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX is
    PORT(
        SEL: in STD_LOGIC_VECTOR(1 downto 0);
        CONST: in STD_LOGIC_VECTOR(7 downto 0);
        --CONST1: in STD_LOGIC_VECTOR()
        DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);
        DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);
    );
end entity MUX;

```

```

        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)
    );
end MUX;

architecture Behavioral of MUX is
begin
    process (SEL, DATA_IN0, DATA_IN1, CONST)
    begin
        if (SEL = "00") then
            OUTPUT <= DATA_IN0;
        elsif (SEL = "01") then
            OUTPUT <= DATA_IN1;
        else
            OUTPUT <= CONST;
        end if;
    end process;
end Behavioral;

```

Файл RAM.vhd:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY RAMTest IS
END RAMTest;

ARCHITECTURE behavior OF RAMTest IS
    COMPONENT RAM
    PORT(
        CLOCK: IN std_logic;
        WR : IN std_logic;
        ADDR : IN std_logic_vector(1 downto 0);
        DATA : IN std_logic_vector(7 downto 0);
        OUTPUT : OUT std_logic_vector(7 downto 0)
    );

```

```

    END COMPONENT;

    signal CLOCK: std_logic := '0';
    signal WR : std_logic := '0';
    signal ADDR : std_logic_vector(1 downto 0) := (others
=> '0');
    signal DATA : std_logic_vector(7 downto 0) := (others
=> '0');
    signal OUTPUT : std_logic_vector(7 downto 0);

BEGIN

    uut: RAM PORT MAP (
        CLOCK => CLOCK,
        WR => WR,
        ADDR => ADDR,
        DATA => DATA,
        OUTPUT => OUTPUT
    );

    clock_proc: process
    begin
        CLOCK <= not CLOCK;
        wait for 1ps;
    end process;

    stim_proc: process
    begin
        WR <= '1';
        ADDR <= "00";
        DATA <= "11111111";
        wait for 2ps;
        WR <= '0';
        assert OUTPUT = DATA report "OUTPUT != DATA when ADDR
= 00 and WR = 0" severity FAILURE;
        DATA <= "00000000";
    end process;

```

```

        wait for 2ps;
        assert OUTPUT = x"FF" report "OUTPUT != x'FF' when
ADDR = 00 and WR = 0" severity FAILURE;
        ADDR <= "01";
        WR <= '1';
        DATA <= x"AF";
        wait for 2ps;
        assert OUTPUT = x"AF" report "OUTPUT != x'AF' when
ADDR = 01 and WR = 1" severity FAILURE;
        wait;
    end process;

END;

```

Файл SEG_DECODER.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity SEG_DECODER is
    port( CLOCK : IN STD_LOGIC;
          RESET : IN STD_LOGIC;
          ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7
DOWNTO 0);
          COMM_ONES          : OUT STD_LOGIC;
          COMM_DECS          : OUT STD_LOGIC;
          COMM_HUNDREDS      : OUT STD_LOGIC;
          SEG_A              : OUT STD_LOGIC;
          SEG_B              : OUT STD_LOGIC;
          SEG_C              : OUT STD_LOGIC;

```

```

        SEG_D      : OUT STD_LOGIC;
        SEG_E      : OUT STD_LOGIC;
        SEG_F      : OUT STD_LOGIC;
        SEG_G      : OUT STD_LOGIC;
        DP         : OUT STD_LOGIC);
end SEG_DECODER;

architecture Behavioral of SEG_DECODER is

    signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) :=
"0000";
    signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) :=
"0001";
    signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0)
:= "0000";

begin
    BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
        variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
        variable bcd      : STD_LOGIC_VECTOR(11 downto 0)
;
    begin
        bcd      := (others => '0') ;
        hex_src  := ACC_DATA_OUT_BUS;

        for i in hex_src'range loop
            if bcd(3 downto 0) > "0100" then
                bcd(3 downto 0) := bcd(3 downto 0) +
"0011" ;
            end if ;
            if bcd(7 downto 4) > "0100" then
                bcd(7 downto 4) := bcd(7 downto 4) +
"0011" ;
            end if ;
            if bcd(11 downto 8) > "0100" then
                bcd(11 downto 8) := bcd(11 downto 8) +

```

```

"0011" ;
        end if ;

        bcd := bcd(10 downto 0) &
hex_src(hex_src'left) ; -- shift bcd + 1 new entry
        hex_src := hex_src(hex_src'left - 1 downto
hex_src'right) & '0' ; -- shift src + pad with 0
        end loop ;

HONDREDS_BUS      <= bcd (11 downto 8);
DECS_BUS          <= bcd (7  downto 4);
ONES_BUS          <= bcd (3  downto 0);

end process BIN_TO_BCD;

INDICATE : process(CLOCK)
    type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

    variable CUR_DIGIT      : DIGIT_TYPE := ONES;
    variable DIGIT_VAL      : STD_LOGIC_VECTOR(3
downto 0) := "0000";
    variable DIGIT_CTRL     : STD_LOGIC_VECTOR(6
downto 0) := "0000000";
    variable COMMONS_CTRL  : STD_LOGIC_VECTOR(2
downto 0) := "000";

    begin
        if (rising_edge(CLOCK)) then
            if(RESET = '0') then
                case CUR_DIGIT is
                    when ONES =>
                        DIGIT_VAL := ONES_BUS;
                        CUR_DIGIT := DECS;
                        COMMONS_CTRL := "001";
                    when DECS =>
                        DIGIT_VAL := DECS_BUS;

```

```

CUR_DIGIT := HUNDREDS;
COMMONS_CTRL := "010";
when HUNDREDS =>
    DIGIT_VAL :=
HONDREDS_BUS;

CUR_DIGIT := ONES;
COMMONS_CTRL := "100";
when others =>
    DIGIT_VAL := ONES_BUS;
CUR_DIGIT := ONES;
COMMONS_CTRL := "000";
end case;

case DIGIT_VAL is

--abcdefg
    when "0000" => DIGIT_CTRL :=
"1111110";
    when "0001" => DIGIT_CTRL :=
"0110000";
    when "0010" => DIGIT_CTRL :=
"1101101";
    when "0011" => DIGIT_CTRL :=
"1111001";
    when "0100" => DIGIT_CTRL :=
"0110011";
    when "0101" => DIGIT_CTRL :=
"1011011";
    when "0110" => DIGIT_CTRL :=
"1011111";
    when "0111" => DIGIT_CTRL :=
"1110000";
    when "1000" => DIGIT_CTRL :=
"1111111";
    when "1001" => DIGIT_CTRL :=
"1111011";
    when others => DIGIT_CTRL :=

```

```

"0000000";

        end case;
    else
        DIGIT_VAL := ONES_BUS;
        CUR_DIGIT := ONES;
        COMMONS_CTRL := "000";
    end if;

    COMM_ONES      <= not
COMMONS_CTRL(0);
    COMM_DECS      <= not
COMMONS_CTRL(1);
    COMM_HUNDREDS <= not COMMONS_CTRL(2);

    SEG_A <= not DIGIT_CTRL(6);
    SEG_B <= not DIGIT_CTRL(5);
    SEG_C <= not DIGIT_CTRL(4);
    SEG_D <= not DIGIT_CTRL(3);
    SEG_E <= not DIGIT_CTRL(2);
    SEG_F <= not DIGIT_CTRL(1);
    SEG_G <= not DIGIT_CTRL(0);
    DP    <= '1';

    end if;
end process INDICATE;

end Behavioral;

```

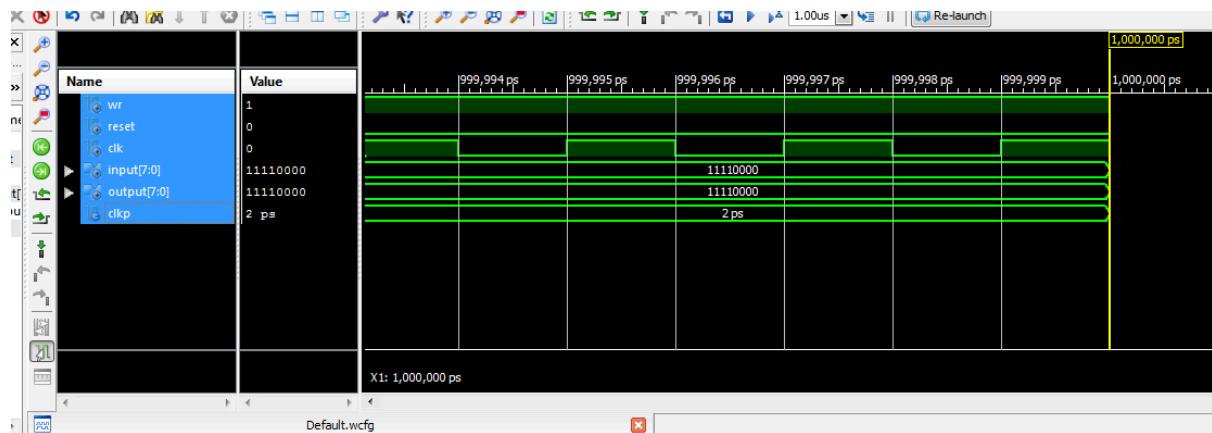



Рис. 3 - часова діаграма ACC

 


Рис. 4 - часова діаграма ALU

 


Рис. 5 - часова діаграма MUX

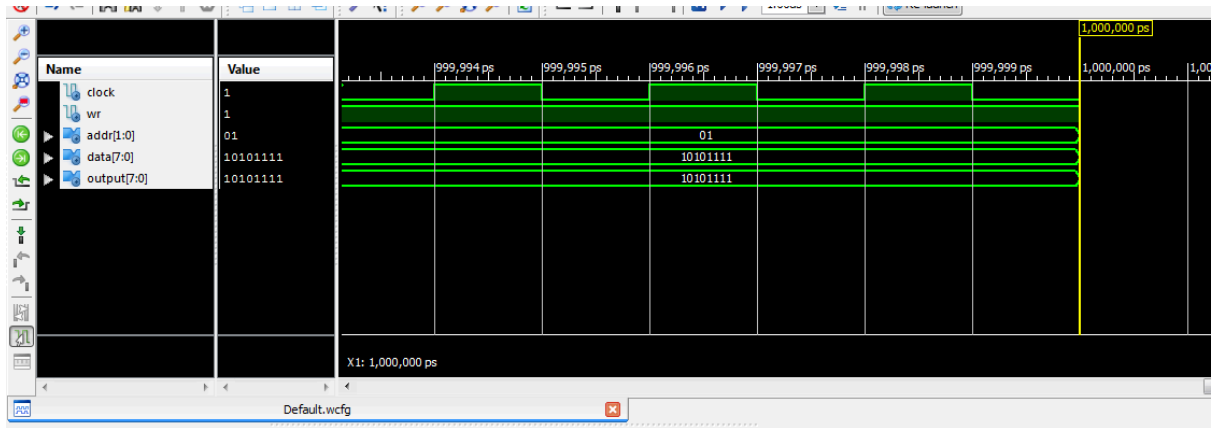


Рис. 6 - часова діаграма RAM

 


Рис. 7 - часова діаграма SEG_DECODER

 


Рис. 8 - часова діаграма TopLevel

Файл TopLevelTest.vhd:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY TopLevel_TopLevel_sch_tb IS
END TopLevel_TopLevel_sch_tb;
ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS

    COMPONENT TopLevel
    PORT( CLOCK:    IN    STD_LOGIC;
          RESET    :    IN    STD_LOGIC;
          ENTER_OP1 :    IN    STD_LOGIC;
          ENTER_OP2 :    IN    STD_LOGIC;
          CALCULATE :    IN    STD_LOGIC;
          DATA_IN  :    IN    STD_LOGIC_VECTOR (7 DOWNTO
0);

          COMMON_0_OUT :    OUT    STD_LOGIC;
          COMMON_1_OUT :    OUT    STD_LOGIC;
          COMMON_2_OUT :    OUT    STD_LOGIC;
          TEST: OUT STD_LOGIC_VECTOR(7 downto 0);
          A_OUT      :    OUT    STD_LOGIC;
          B_OUT      :    OUT    STD_LOGIC;
          C_OUT      :    OUT    STD_LOGIC;
          D_OUT      :    OUT    STD_LOGIC;
          E_OUT      :    OUT    STD_LOGIC;
          F_OUT      :    OUT    STD_LOGIC;
          G_OUT      :    OUT    STD_LOGIC;
          DP_OUT     :    OUT    STD_LOGIC;
          RAMOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
          ALUOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
          RAMA: OUT STD_LOGIC_VECTOR(1 downto 0);
          RAMWR: OUT STD_LOGIC;
          OVERFLOW :    OUT    STD_LOGIC);

```

```

END COMPONENT;

SIGNAL CLOCK      :   STD_LOGIC := '0';
SIGNAL RESET      :   STD_LOGIC;
SIGNAL ENTER_OP1   :   STD_LOGIC;
SIGNAL ENTER_OP2   :   STD_LOGIC;
SIGNAL CALCULATE   :   STD_LOGIC;
SIGNAL DATA_IN    :   STD_LOGIC_VECTOR (7 DOWNTO 0);
SIGNAL COMMON_0_OUT :   STD_LOGIC;
SIGNAL COMMON_1_OUT :   STD_LOGIC;
SIGNAL COMMON_2_OUT :   STD_LOGIC;
SIGNAL A_OUT       :   STD_LOGIC;
SIGNAL B_OUT       :   STD_LOGIC;
SIGNAL C_OUT       :   STD_LOGIC;
SIGNAL D_OUT       :   STD_LOGIC;
SIGNAL E_OUT       :   STD_LOGIC;
SIGNAL F_OUT       :   STD_LOGIC;
SIGNAL G_OUT       :   STD_LOGIC;
SIGNAL DP_OUT      :   STD_LOGIC;
SIGNAL OVERFLOW    :   STD_LOGIC;
    SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);
    SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal ALUOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMA: STD_LOGIC_VECTOR(1 downto 0);
    signal RAMWR: STD_LOGIC;

--    constant CLOCK_period : time := 166ns;
    constant CLKP: time := 12ms;--24ms;

BEGIN

    UUT: TopLevel PORT MAP(
        CLOCK => CLOCK,
        RESET => RESET,
        ENTER_OP1 => ENTER_OP1,

```

```

        ENTER_OP2 => ENTER_OP2,
        CALCULATE => CALCULATE,
        DATA_IN => DATA_IN,
        COMMON_0_OUT => COMMON_0_OUT,
        COMMON_1_OUT => COMMON_1_OUT,
        COMMON_2_OUT => COMMON_2_OUT,
        A_OUT => A_OUT,
        B_OUT => B_OUT,
        C_OUT => C_OUT,
        D_OUT => D_OUT,
        E_OUT => E_OUT,
        F_OUT => F_OUT,
        G_OUT => G_OUT,
        DP_OUT => DP_OUT,
        OVERFLOW => OVERFLOW,
        TEST => TEST,
        RAMOUT => RAMOUT,
        ALUOUT => ALUOUT,
        RAMA => RAMA,
        RAMWR => RAMWR
    );

    CLOCK_process: process
    begin
        CLOCK <= '0';
        wait for 83ns;
        CLOCK <= '1';
        wait for 83ns;
    end process;

-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    lp1: for i in 4 to 4 loop
        lp2: for j in 2 to 2 loop
            TEST2 <=

```

```

std_logic_vector((to_unsigned(i * j, 8) srl 1) + i + 10);
    ENTER_OP1 <= '1';
    ENTER_OP2 <= '1';
    CALCULATE <= '1';
    DATA_IN <= (others => '0');
    RESET <= '0';
    wait for CLKP;
    RESET <= '1';
    wait for CLKP;
    DATA_IN <=
std_logic_vector(to_unsigned(i, 8)); -- A
    ENTER_OP1 <= '0';
    wait for CLKP;
    ENTER_OP1 <= '1';
    wait for CLKP;
    DATA_IN <=
std_logic_vector(to_unsigned(j, 8)); -- B
    ENTER_OP2 <= '0';
    wait for CLKP;
    ENTER_OP2 <= '1';
    wait for CLKP;
    CALCULATE <= '0'; -- START CALCULATION
    wait for CLKP* 7;
    assert TEST = TEST2 severity FAILURE;
    wait for CLKP;
        end loop;
    end loop;

    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***

END;
```

 


Рис. 9 - семисегментний індикатор

Вхідне число: $020_{10} = 10100_2$

Сотні: $g = 1$ ($a, b, c, d, e, f = 0$)

Десятки: $c = 1, f = 1$ ($a, b, d, e, g = 0$)

Одиниці: $g = 1$ ($a, b, c, d, e, f = 0$)

Висновок: виконуючи дану неймовірну лабораторну роботу та оформлюючи звіт до неї, я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.